

Week 2: Electronic filters, the mechanical domain, and equivalent circuits

Microphone and Loudspeaker Design - Level 5

Joshua Meggitt

Acoustics Research Centre, University of Salford

What are we covering today?

1. A quick recap...
2. Electrical filters
3. Equivalent circuits
4. Mechanical domain
5. Impedance analogy
6. Mobility analogy

A weekly fact about Salford..!

Did you know...

- In 1850, under the terms of the Museums Act 1845, the Salford council established the Royal Museum and Public Library; the first unconditional free public library in World! The library sits at the head of Peel park and is now the Salford Museum and Art Gallery.

A quick recap...

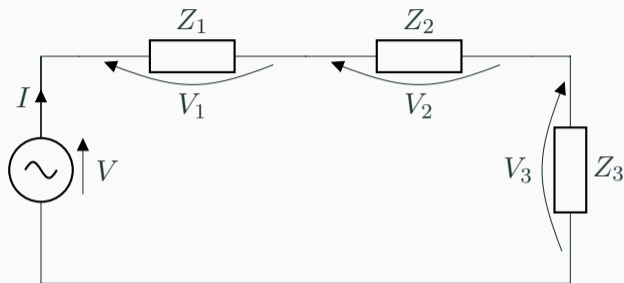


Figure 1: Three arbitrary impedances in series

- For a **series arrangement**, the total impedance Z_T presented by the circuit is,

$$Z_T = Z_1 + Z_2 + Z_3. \quad (1)$$

AC circuit theory - recap

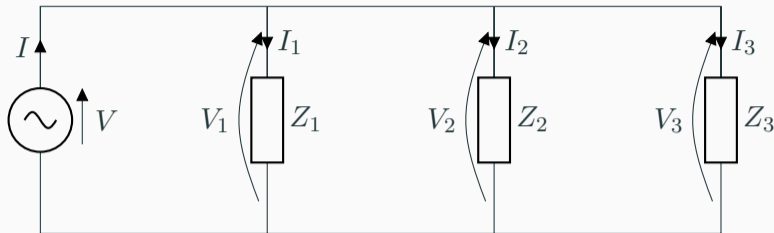


Figure 2: Three arbitrary impedances in parallel

- For a **parallel arrangement**, the total impedance Z_T presented by the circuit is,

$$Z_T = \left(\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} \right)^{-1}. \quad (2)$$

- For **two elements** in parallel:

$$Z_T = \frac{Z_1 Z_2}{Z_1 + Z_2}. \quad (3)$$

Voltage and current dividers

- Voltage divider transfer function

$$H = \frac{V_{out}}{V_{in}} = \frac{Z_{out}}{Z_T} \rightarrow \frac{Z_2}{Z_1 + Z_2} \quad (4)$$

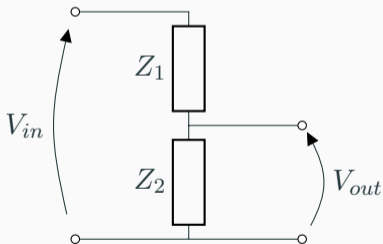


Figure 3: Potential (voltage) divider circuit

- Current divider transfer function

$$H_n = \frac{I_n}{I_T} = \frac{Z_T}{Z_n} \quad (5)$$

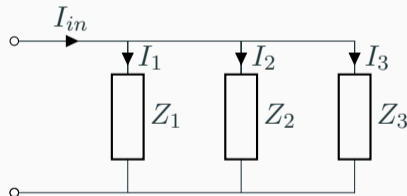


Figure 4: Current divider circuit

Types of component: summary

- Impedance is frequency dependant!

- Resistors

$$Z_{Er} = R \quad (6)$$

- Capacitors

$$Z_{Ec} = \frac{1}{j\omega C} \quad (7)$$

- Inductors

$$Z_{El} = j\omega L \quad (8)$$

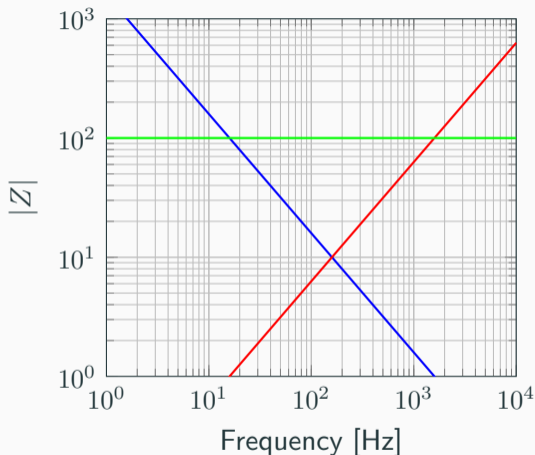


Figure 5: Impedance curves for resistor, capacitor and inductor.

Electrical filters

RC circuit

- Use potential divider rule

$$V_{out} = \frac{Z_C}{Z_R + Z_C} V_{in} \quad (9)$$

- Use component impedances

$$\frac{V_{out}}{V_{in}} = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{1}{j\omega RC + 1} \quad (10)$$

- Take magnitude

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{\sqrt{1 + (\omega RC)^2}} \quad (11)$$

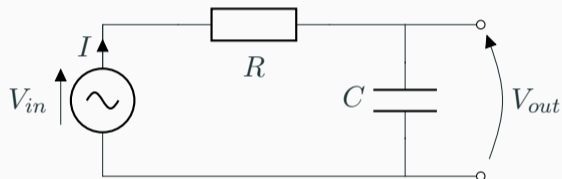


Figure 6: RC circuit

RC circuit

- Transfer function magnitude:

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{\sqrt{1 + (\omega RC)^2}} \quad (12)$$

- In the limit that $\omega \rightarrow 0$

$$\left| \frac{V_{out}}{V_{in}} \right| \rightarrow 1 \quad (13)$$

- In the limit that $\omega \rightarrow \infty$

$$\left| \frac{V_{out}}{V_{in}} \right| \rightarrow 0 \quad (14)$$

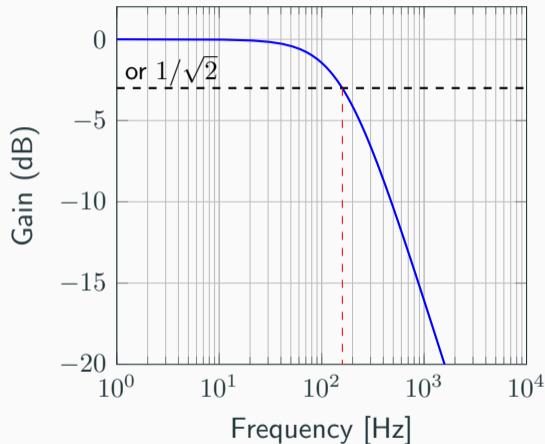


Figure 7: Gain response for an RC circuit, output taken across capacitor.

RC circuit

- The cut-off frequency (ω_c) is when the power output is half that of the input (gain of $1/\sqrt{2}$ or -3dB)

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{\sqrt{2}} = \frac{1}{\sqrt{1 + (\omega_c RC)^2}} \quad (15)$$

- This will happen when $(\omega_c RC)^2 = 1$.
Hence, we can see that,

$$\omega_c = \frac{1}{RC} \quad (16)$$

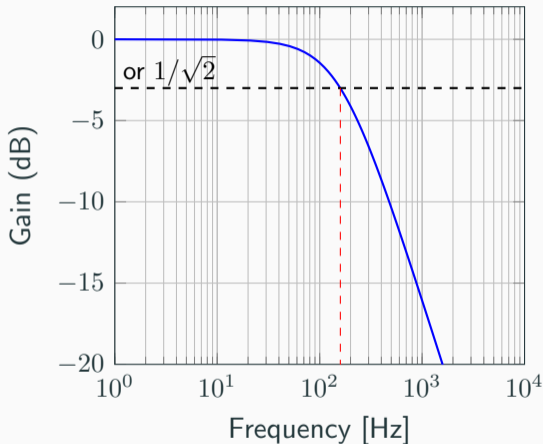


Figure 7: Gain response for an RC circuit, output taken across capacitor.

RC circuit

- Re-parametrise transfer function

$$\frac{V_{out}}{V_{in}} = \frac{1}{j\omega RC + 1} = \frac{1}{j\frac{\omega}{\omega_c} + 1} \quad (17)$$

- The gain at cut off (when $\omega = \omega_c$) is

$$\frac{V_{out}}{V_{in}} = \frac{1}{j + 1} = \frac{1 - j}{2} = \frac{1}{2} - \frac{j}{2} \quad (18)$$

- Using trigonometry, the phase response at cut-off is,

$$\phi = \tan^{-1} \left(\frac{-0.5}{0.5} \right) \rightarrow -45^\circ \quad (19)$$

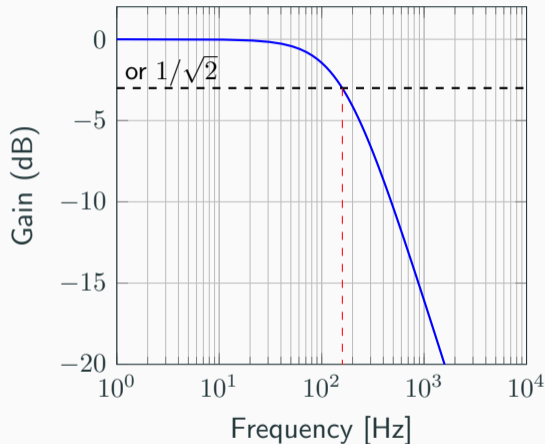


Figure 7: Gain response for an RC circuit, output taken across capacitor.

RL circuit

- Use potential divider rule

$$V_{out} = \frac{Z_L}{Z_R + Z_L} V_{in} \quad (20)$$

- Use component impedances

$$\frac{V_{out}}{V_{in}} = \frac{j\omega L}{R + j\omega L} = \frac{1}{\frac{R}{j\omega L} + 1} \quad (21)$$

- Take magnitude

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{\sqrt{\left(\frac{R}{\omega L}\right)^2 + 1}} \quad (22)$$

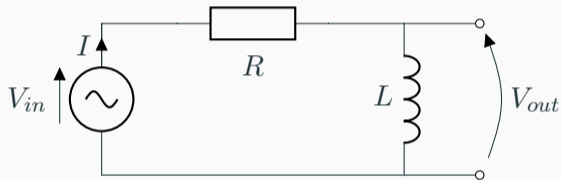


Figure 8: RL circuit

RL circuit

- Transfer function magnitude:

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{\sqrt{\left(\frac{R}{\omega L}\right)^2 + 1}} \quad (23)$$

- In the limit that $\omega \rightarrow 0$

$$\left| \frac{V_{out}}{V_{in}} \right| \rightarrow 0 \quad (24)$$

- In the limit that $\omega \rightarrow \infty$

$$\left| \frac{V_{out}}{V_{in}} \right| \rightarrow 1 \quad (25)$$

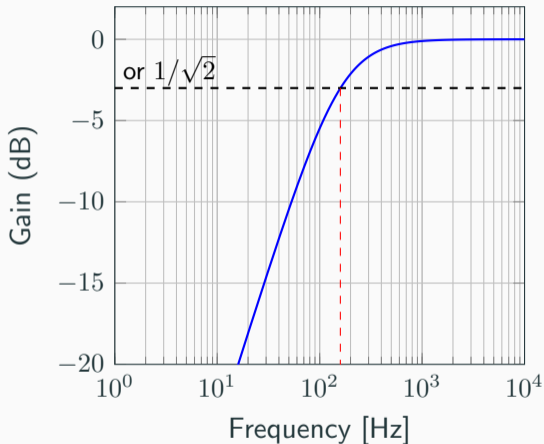


Figure 9: Gain response for an RL circuit, output taken across capacitor.

RL circuit

- The cut-off frequency (ω_c) is when the power output is half that of the input (gain of $1/\sqrt{2}$ or -3dB)

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{\sqrt{2}} = \frac{1}{\sqrt{\left(\frac{R}{\omega_c L}\right)^2 + 1}}. \quad (26)$$

- This will happen when $\left(\frac{R}{\omega_c L}\right)^2 = 1$.
Hence, we can see that,

$$\omega_c = \frac{R}{L}. \quad (27)$$

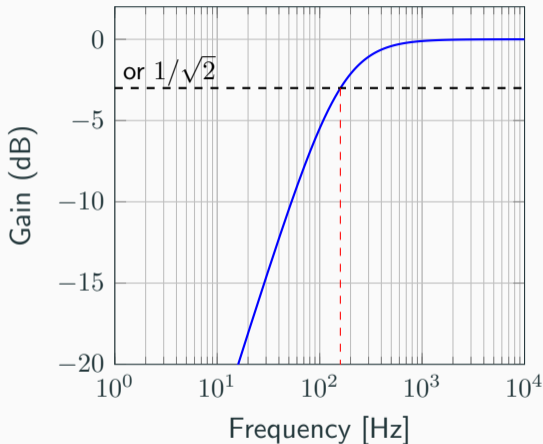


Figure 9: Gain response for an RL circuit, output taken across capacitor.

RL circuit

- Re-parametrise transfer function

$$\frac{V_{out}}{V_{in}} = \frac{1}{\frac{R}{j\omega L} + 1} = \frac{1}{1 - j\frac{\omega_c}{\omega}} \quad (28)$$

- The gain at cut off (when $\omega = \omega_c$) is

$$\frac{V_{out}}{V_{in}} = \frac{1}{1 - j} = \frac{1}{2} + \frac{j}{2} \quad (29)$$

- Using trigonometry, the phase response at cut-off is,

$$\phi = \tan^{-1} \left(\frac{0.5}{0.5} \right) \rightarrow 45^\circ. \quad (30)$$

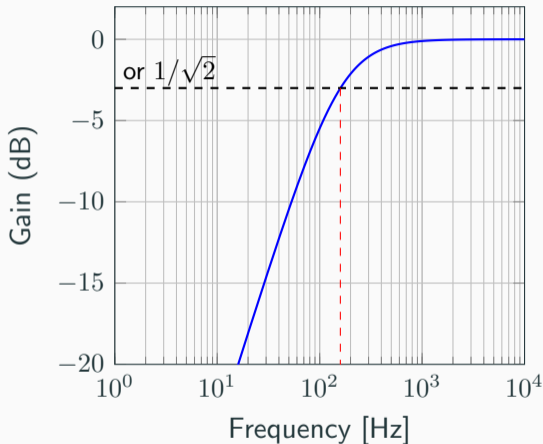


Figure 9: Gain response for an RL circuit, output taken across capacitor.

LCR circuit

- Total impedance

$$Z_{LCR} = R + j\omega L + \frac{1}{j\omega C} \quad (31)$$

- Use potential divider rule

$$V_{out} = \frac{Z_R}{Z_R + Z_L + Z_C} V_{in} \quad (32)$$

- Use component impedances

$$\frac{V_{out}}{V_{in}} = \frac{R}{R + j\omega L + \frac{1}{j\omega C}} = \frac{1}{1 + \frac{j\omega L}{R} + \frac{1}{j\omega RC}} \quad (33)$$

- Take magnitude

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{\sqrt{1 + \left(\frac{\omega L}{R} - \frac{1}{\omega RC} \right)^2}} \quad (34)$$

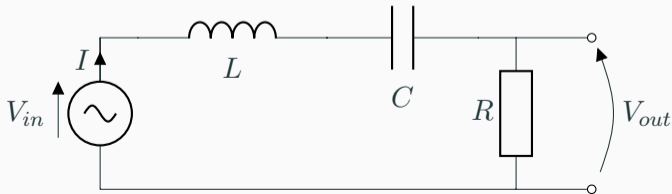


Figure 10: LCR circuit

LCR circuit

- Transfer function magnitude:

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{\sqrt{1 + \left(\frac{\omega L}{R} - \frac{1}{\omega RC} \right)^2}} \quad (35)$$

- In the limit that $\omega \rightarrow 0$

$$\left| \frac{V_{out}}{V_{in}} \right| \rightarrow 0 \quad (\text{Det. by capacitance}) \quad (36)$$

- In the limit that $\omega \rightarrow \infty$

$$\left| \frac{V_{out}}{V_{in}} \right| \rightarrow 0 \quad (\text{Det. by inductance}) \quad (37)$$

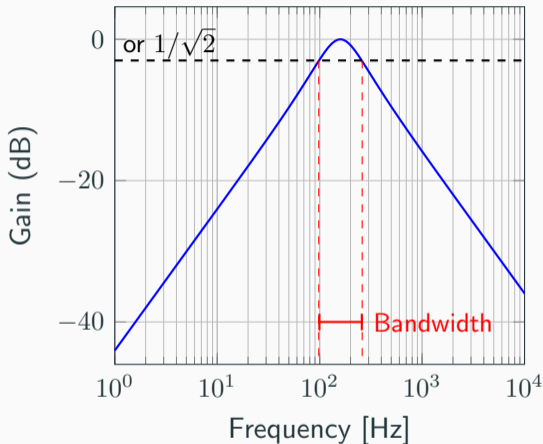


Figure 11: Gain response for an LCR circuit, output taken across resistor.

LCR circuit

- Maximum gain when,

$$\left(\frac{\omega L}{R} - \frac{1}{\omega RC} \right) = 0 \quad (38)$$

- Rearrange to find resonant frequency

$$\omega_r = \frac{1}{\sqrt{LC}} \quad (39)$$

- The BW and resonant frequency determine the Q-Factor

$$Q = \frac{\omega_r}{BW} = \frac{1}{\sqrt{LC}} \frac{L}{R} = \frac{1}{R} \sqrt{\frac{L}{C}} \quad (40)$$

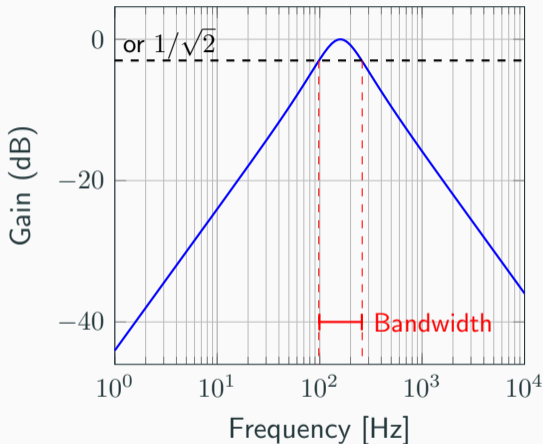


Figure 11: Gain response for an LCR circuit, output taken across resistor.

Impedance: a common language

- **Electrical impedance** is the measure of the opposition that a circuit presents to a current when a voltage is applied

$$Z_E = \frac{V}{I} \quad (41)$$

- **Mechanical impedance** is a measure of how much a structure resists motion (velocity) when subjected to a force

$$Z_M = \frac{F}{u} \quad (42)$$

- **Acoustic impedance** is a measure of the opposition that a system presents to the acoustic flow (volume velocity) when subjected to acoustic pressure

$$Z_A = \frac{p}{U} \quad (43)$$

Impedance: resistance vs. reactance

- Impedance is generally a complex quantity. It has a real part and an imaginary part.

$$Z = R + jX \quad (44)$$

- Real part is called the resistance - R
 - Imaginary part is called reactance - X
- Resistance describes energy loss (e.g. through heat, friction, etc.)
- Reactance describes energy storage (e.g. through mag/elec fields, momentum, etc.)

Equivalent circuits

Equivalent circuits: drop and flow

- We have covered 3 key electrical components: resistor, capacitor, inductor.
- There are three generic quantities:
 1. The (voltage) drop across the (electrical) component
 2. The (current) flow through the (electrical) component
 3. The magnitude of the (electrical) component itself (resistance, capacitance, inductance)
- These generic quantities are not limited to electrical components:
 - For a mechanical system we have force (F) and velocity (u)
 - For an acoustic system we have pressure (p) and volume velocity (U)
 - But which quantity is the drop and which is the flow? - **Depends on the problem!**

Mechanical domain

Mechanical domain: three main components

- Three main components: mass elements, springs, and dampers

- Mechanical impedance:

$$Z_M = \frac{F}{u} \quad (45)$$

- Turn out to be very similar to those of electrical components discussed so far.

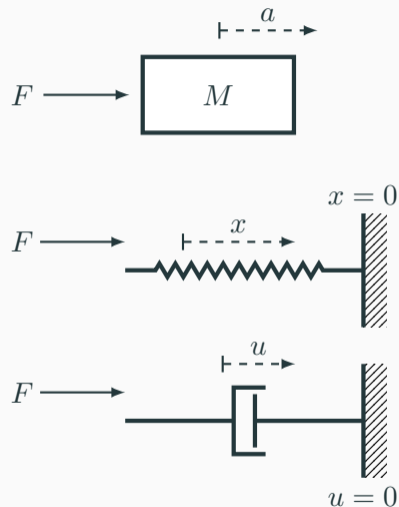


Figure 12: Mass, spring and damper. 21

Mechanical domain: mass

- Newton's 2nd Law

$$F = Ma \quad (46)$$

- Assume periodic force $F = F_o e^{j\omega t}$

$$F = M \frac{du}{dt} = j\omega M u \quad (47)$$

- The impedance is then,

$$Z_M = \frac{F}{u} = j\omega M \quad (48)$$

- Impedance is proportional to frequency and complex - what electrical component does this look like?



Figure 13: Mass element.

Mechanical domain: spring

- Hooke's Law

$$F = kx = \frac{1}{C}x \quad (49)$$

- Assume periodic force $F = F_o e^{j\omega t}$

$$F = \frac{1}{C} \int u dt = \frac{1}{j\omega C} u \quad (50)$$

- The impedance is then,

$$Z_C = \frac{F}{u} = \frac{1}{j\omega C} \quad (51)$$

- Impedance is inv. prop. to freq. and complex -
what elec. component does this look like?

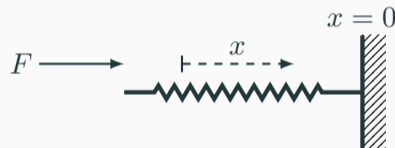


Figure 14: Spring element.

Mechanical domain: damper

- Viscous damping element

$$F = Ru \quad (52)$$

- The impedance is then,

$$Z_R = \frac{F}{u} = R \quad (53)$$

- Impedance is constant wrt frequency and real -
what electrical component does this look like?

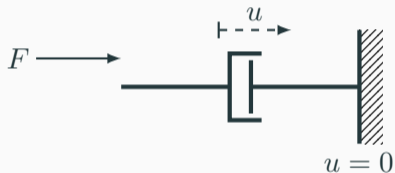


Figure 15: Damping element.

Impedance analogy

Equivalent circuits: drop and flow

- For the **impedance analogy** we think of:
 - Force as being analogous to voltage $F \rightarrow V$
 - Velocity as being analogous to current $u \rightarrow I$
- By drawing this particular equivalence we preserve the analogy between mechanical and electrical impedance:

$$Z_M \rightarrow Z_E \quad (54)$$

- But, the topology of our problem is lost... i.e. mechanical system is arranged differently to its analogous electrical circuit
- Another popular one is called the mobility analogy...

Impedance analogy: summary

Element	Impedance analogy	Mobility analogy
Mass	Mass \leftrightarrow Inductor $Z_M = j\omega M_M \leftrightarrow Z_E = j\omega L_E$	
Spring	Spring \leftrightarrow Capacitor $Z_M = \frac{1}{j\omega C_M} \leftrightarrow Z_E = \frac{1}{j\omega C_E}$	
Damper	Damper \rightarrow Resistor $Z_M = R_M \leftrightarrow Z_E = R_E$	

Impedance analogy: mass-spring-damper

- Use analogy between mechanical and electrical components to model mechanical systems as electric circuits.
- To draw equivalent circuit first recall the definition of impedance analogy:

$$F \rightarrow V \quad u \rightarrow I \quad (55)$$

- Note that the mass, spring and damper all have the same velocity, because they are connected together...

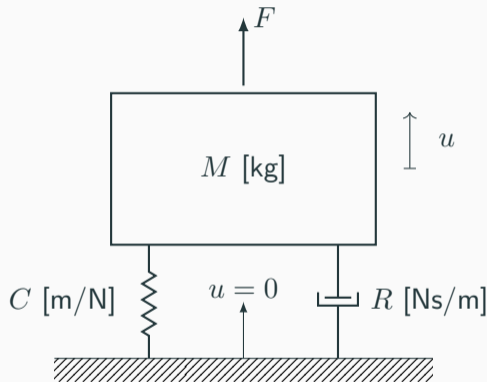


Figure 16: Mass-spring-damper.

Impedance analogy: mass-spring-damper

- Using AC circuit theory we can easily calculate the impedance of the mechanical system,

$$Z_M = j\omega M_M + \frac{1}{j\omega C_M} + R_M \quad (56)$$

- Mechanical velocity given by,

$$u = \frac{F}{Z_M} = \frac{F}{j\omega M_M + \frac{1}{j\omega C_M} + R_M} \quad (57)$$

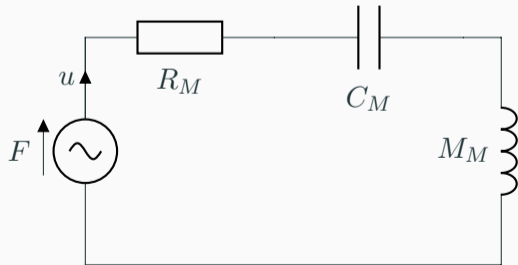


Figure 17: Mass-spring-damper equivalent circuit

Impedance analogy: mass-spring-damper

- Using equivalent circuit we can calculate the velocity of the mass,

$$u = \frac{F}{j\omega M_M + \frac{1}{j\omega C_M} + R_M} \quad (58)$$

- As expected, the response looks just like an LCR circuit!

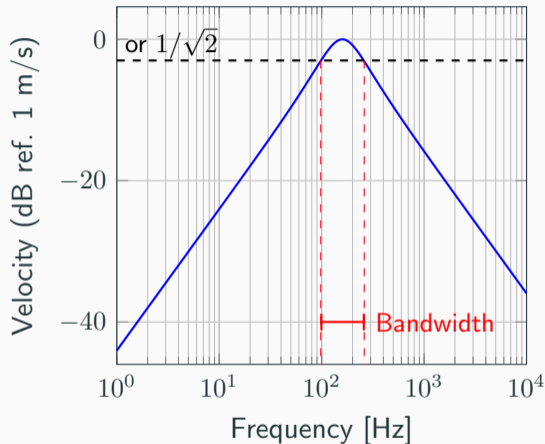


Figure 11: Velocity response of a mass-spring system.

Mobility analogy

- For the **impedance analogy** we made the following equivalences:
 - Force as being analogous to voltage $F \rightarrow V$ (drop parameter)
 - Velocity as being analogous to current $u \rightarrow I$ (flow parameter)
- But there is no reason why we cant consider the opposite!
- For the **mobility analogy** we make the following equivalences:
 - Force as being analogous to current $F \rightarrow I$ (flow parameter)
 - Velocity as being analogous to voltage $u \rightarrow V$ (drop parameter)

Next week...

- Mobility analogy
- Impedance stuff
- Q-factor
- Reading:
 - Mechanical domain: lecture notes, chp. 4, pg. all
 - Impedance and mobility analogies: lecture notes, chp. 4 pg. all